

## Sensor-less 3-phase BLDC Drive, TIDA-00274

This sensor-less drive design works on the principle of integrating the back-emf of the unexcited motor phase to determine commutation. To demonstrate the effectiveness of the sensor-less control scheme used in this design, the following parameters were verified in this test report. The first two were done with 3 different motors at different speeds at 24V.

- Commutation accuracy: This is a measure of how accurately phase voltage transitions match Hall signals transitions.
- Flutter: This is a measure of rotational speed jitter, and it measures the edge variation of a periodic signal generated by the motor. It is measured from Hall signals as the ratio of the max-to-min vs mean frequency of one Hall signal.
- Power handling capacity: This is performed at 48V, to test maximum power of the design.


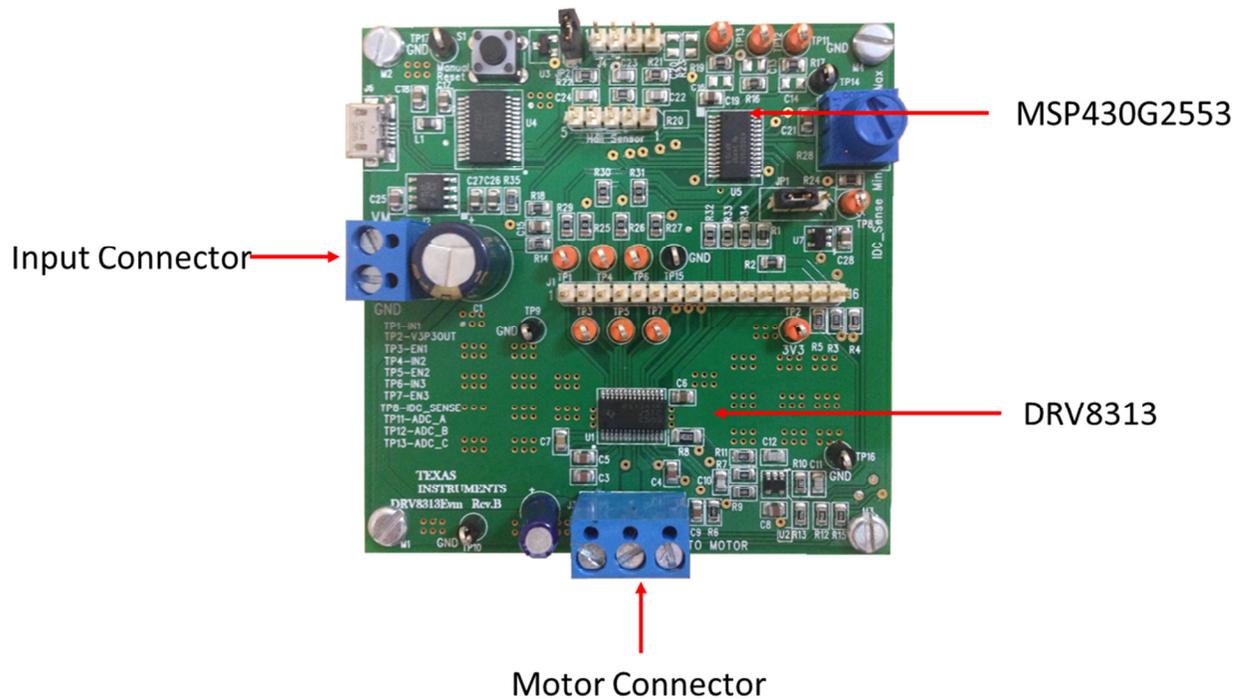



Figure 1: DRV8313 Reference design Circuit Card Assembly

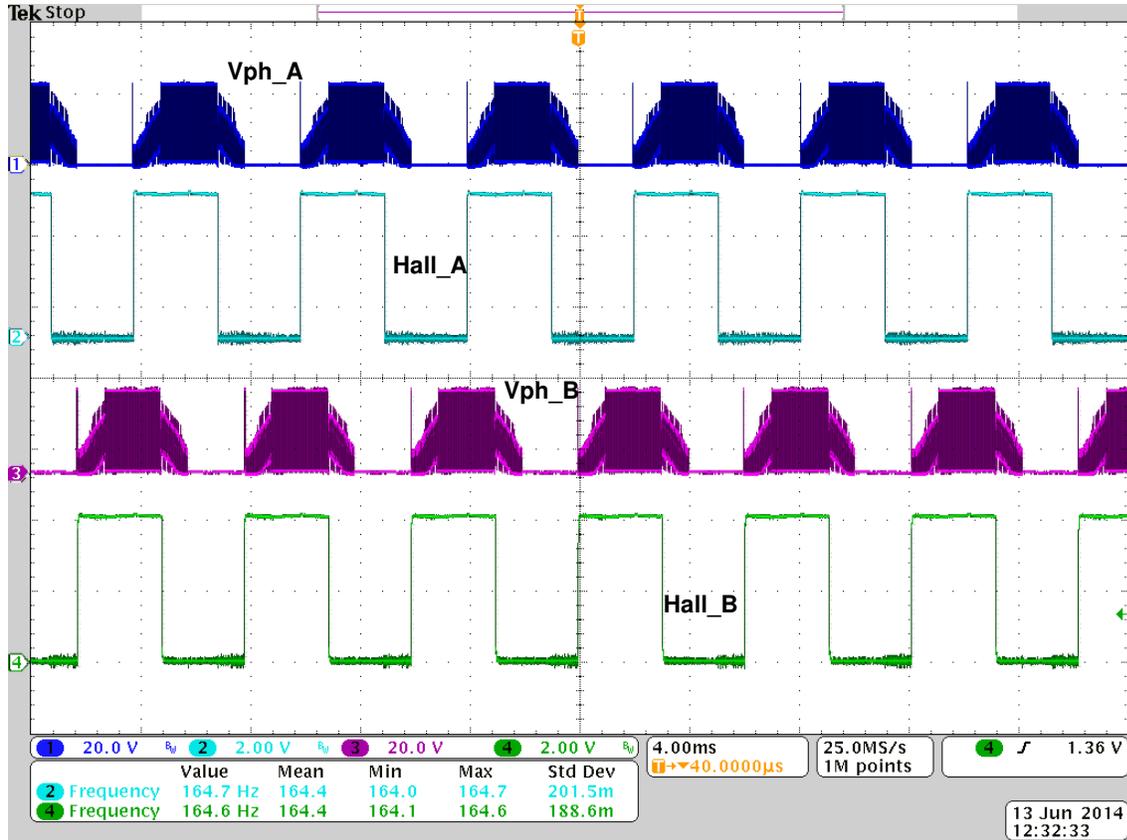

**Figure 2: Motor Phase Voltage with respect to Hall-sensor for Test Motor-1**


- Motor poles-8
- Average speed during test:  $164.4 \times 120 / 8 = 2466 \text{rpm}^1$
- % flutter as per Hall-A:  $(164.7 - 164) / 164.4 \times 100 = 0.43\%$
- % flutter as per Hall-B:  $(164.6 - 164.1) / 164.4 \times 100 = 0.3\%$
- Average flutter: 0.37 %

<sup>1</sup> Speed in Rpm =  $(120 \times \text{Hz} / \text{motor-pole})$

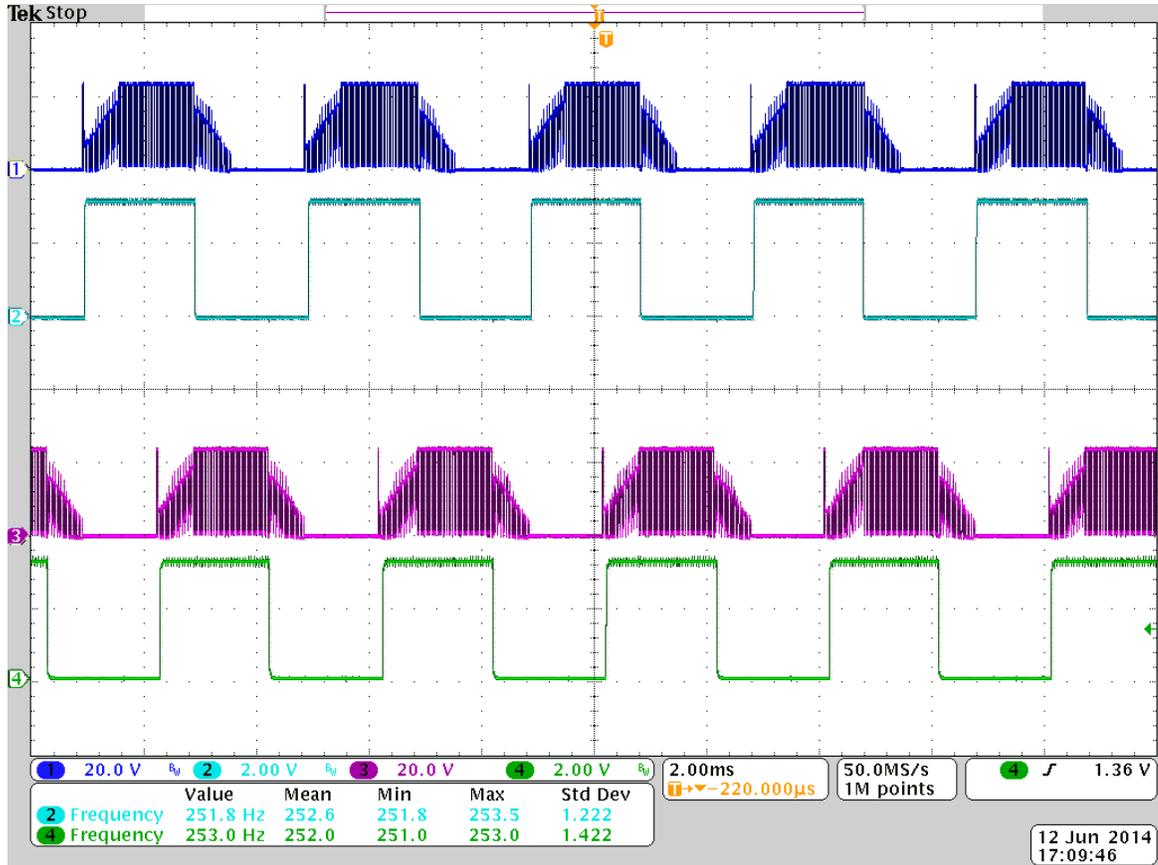

**Figure 3: Motor Phase Voltage with respect to Hall-sensor for Test Motor-2**

- Motor poles-8
- Average speed during test:  $252.3 \times 120 / 8 = 3780 \text{rpm}$
- % flutter as per Hall-A:  $(253.5 - 252.6) / 251.8 \times 100 = 0.67\%$
- % flutter as per Hall-B:  $(253.0 - 250.0) / 252 \times 100 = 0.79\%$
- Average flutter: 0.73%

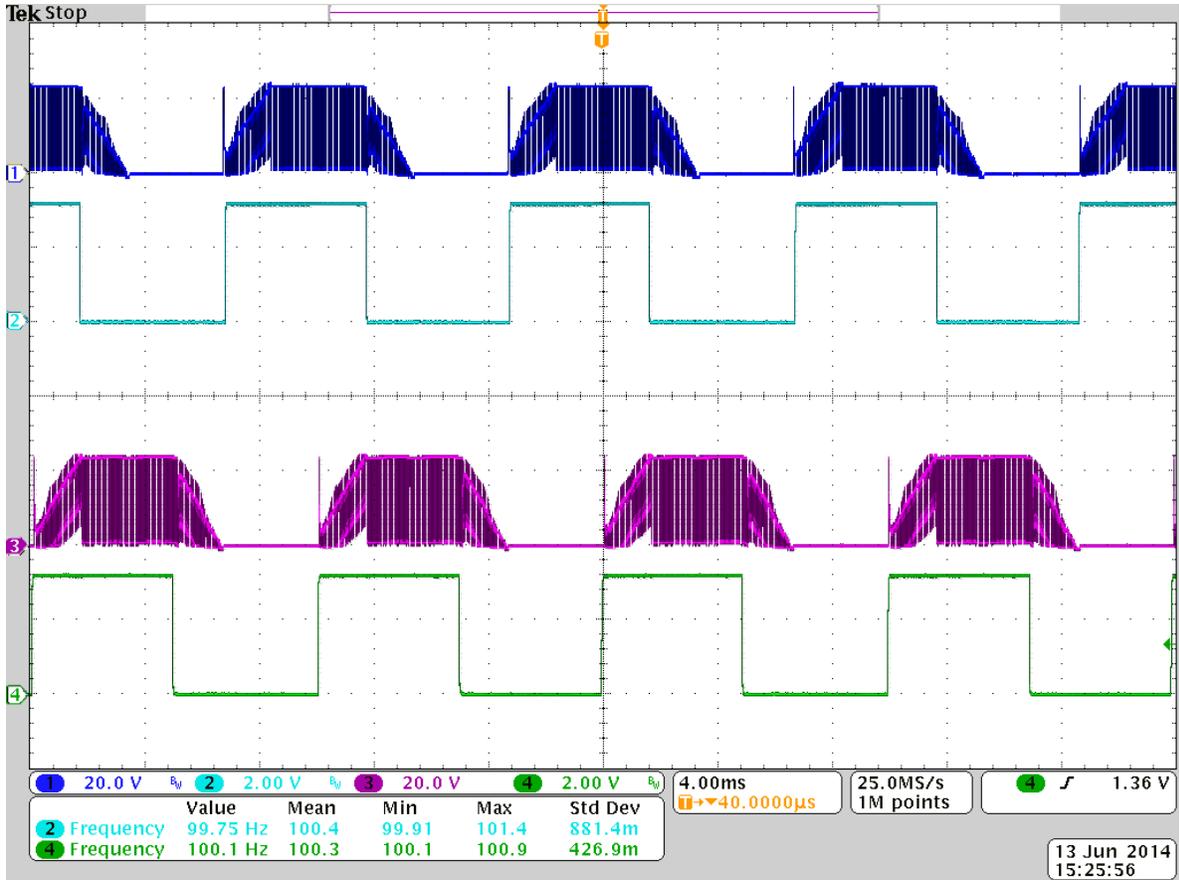

**Figure 4: Motor Phase Voltage with respect to Hall-sensor for Test Motor-3**

- Motor poles-8
- Average speed during test:  $100.35 \times 120 / 8 = 1505 \text{rpm}$
- % flutter as per Hall-A:  $(101.4 - 99.91) / 100.4 \times 100 = 1.48\%$
- % flutter as per Hall-B:  $(100.9 - 100.1) / 100.3 \times 100 = 0.8\%$
- Average flutter: 1.1 %


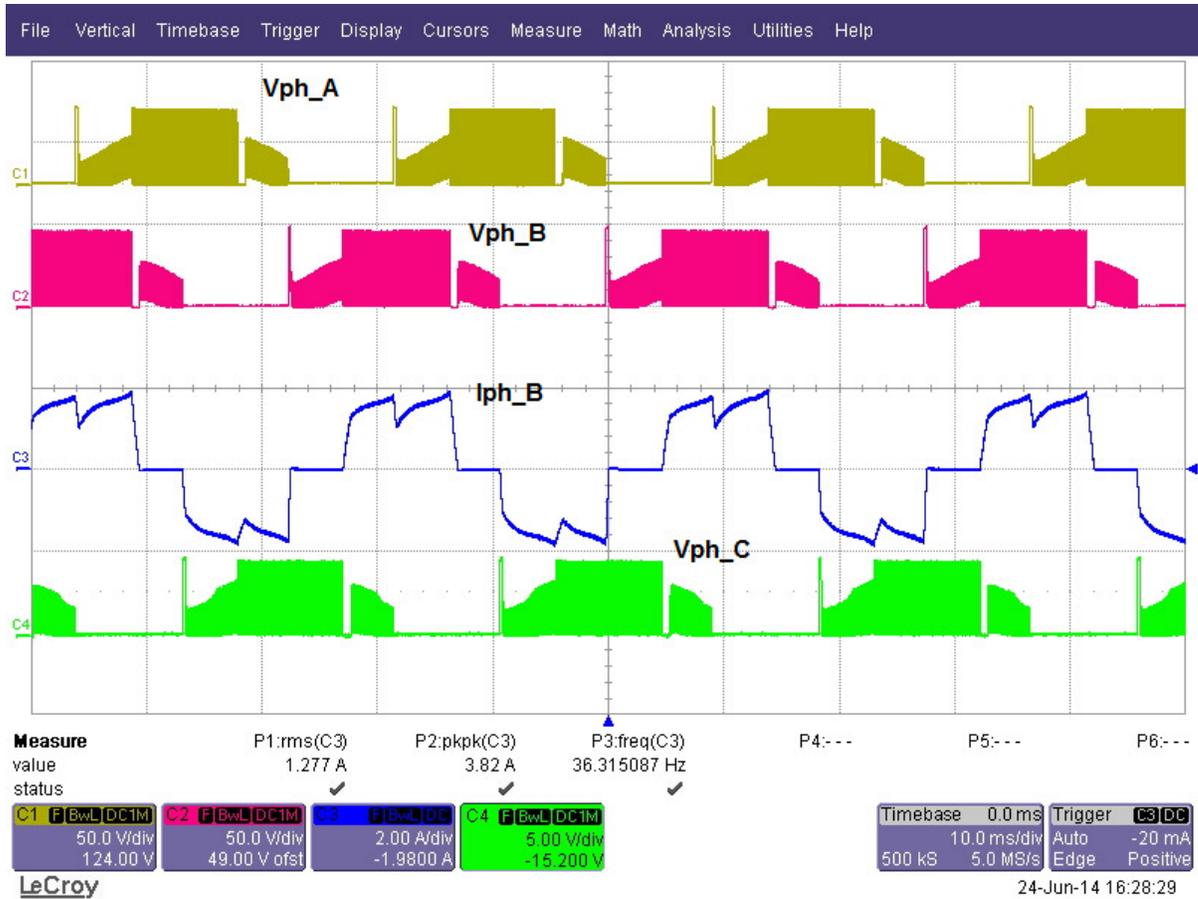


Figure 5: 3-Phase output voltages and phase current at 48Vdc/0.75Adc input

- Motor poles-16
- Average speed during test:  $36.3 \times 120 / 16 = 272\text{rpm}$
- Motor phase current – 1.27Arms/1.9Apk
- Power Input = 36 watt

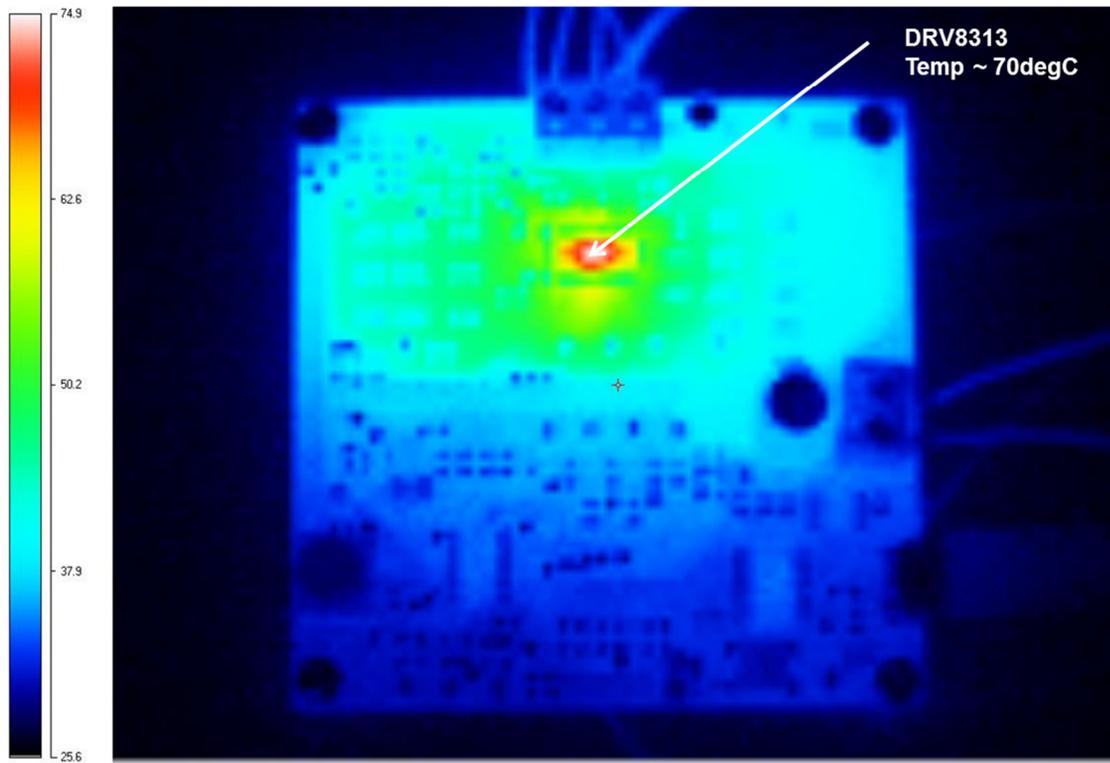

**Figure 6: Thermal image at 48Vdc/0.75Adc, Pin =36Watts**

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated