



Texas Instruments

PMP4442 Test Procedure

China Power Reference Design


REV A

11/12/2014

1 GENERAL

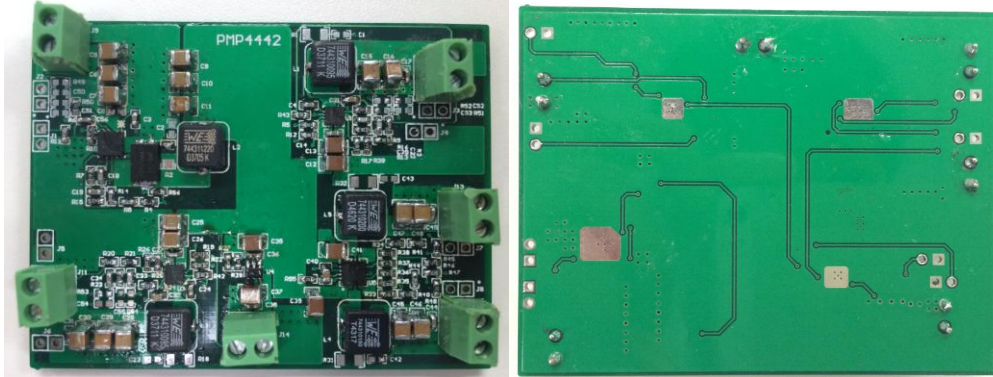1.1 PURPOSE

To provide detailed data for evaluating and verifying the PMP4442, which uses TI new TPS54561-Q1,TPS54388-Q1,TPS57114-Q1,LM26420-Q1,TLV70030-Q1 with size L*W:75mmx58mm. This design is for automotive with 2.1MHz switching frequency in order to avoid the AM band for radio.



1.2 REFERENCE DOCUMENTATION

Schematic PMP4442_SCH.PDF

PMP4442_PCB.PDF

BOM

1.3 TEST EQUIPMENTS

Multi-meter(current): Fluke 8845A


Multi-meter(voltage): Fluke 187

DC Source: Chroma 61530

Electronic load: Chroma 63110A module

Testing demoboard

1.4 SYSTEM BLOCK DIAGRAM

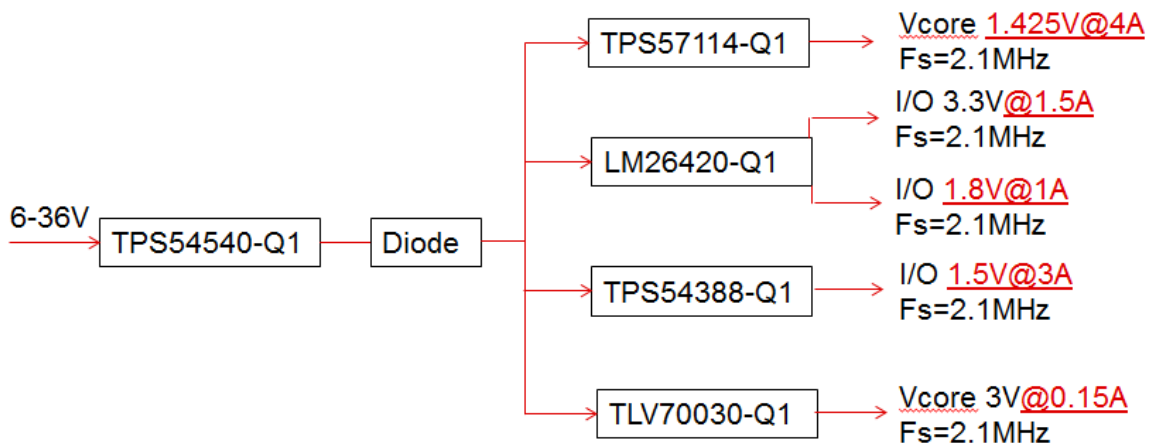


2 Output Characteristics


2.1 TPS54561 for 5V/4A

2.1.1 Output regulation and curve:

12V	Output Current(A)	Output Voltage(V)
	No load	5.057
	0.50	5.051
	1.00	5.049
	1.50	5.048
	2.00	5.047
	2.50	5.046
	3.00	5.045
	3.50	5.044
	4.00	5.042

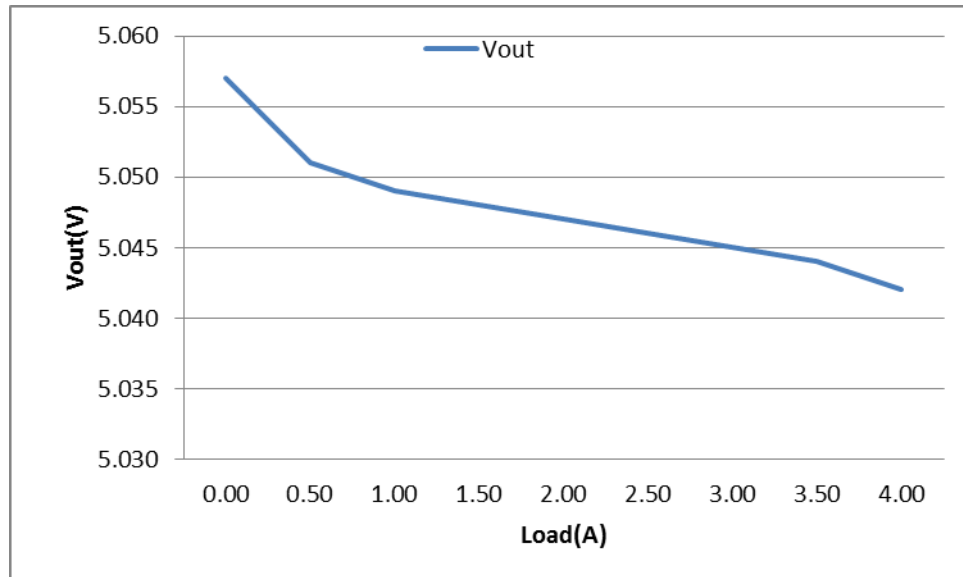


2.1.2 Output ripple voltage:

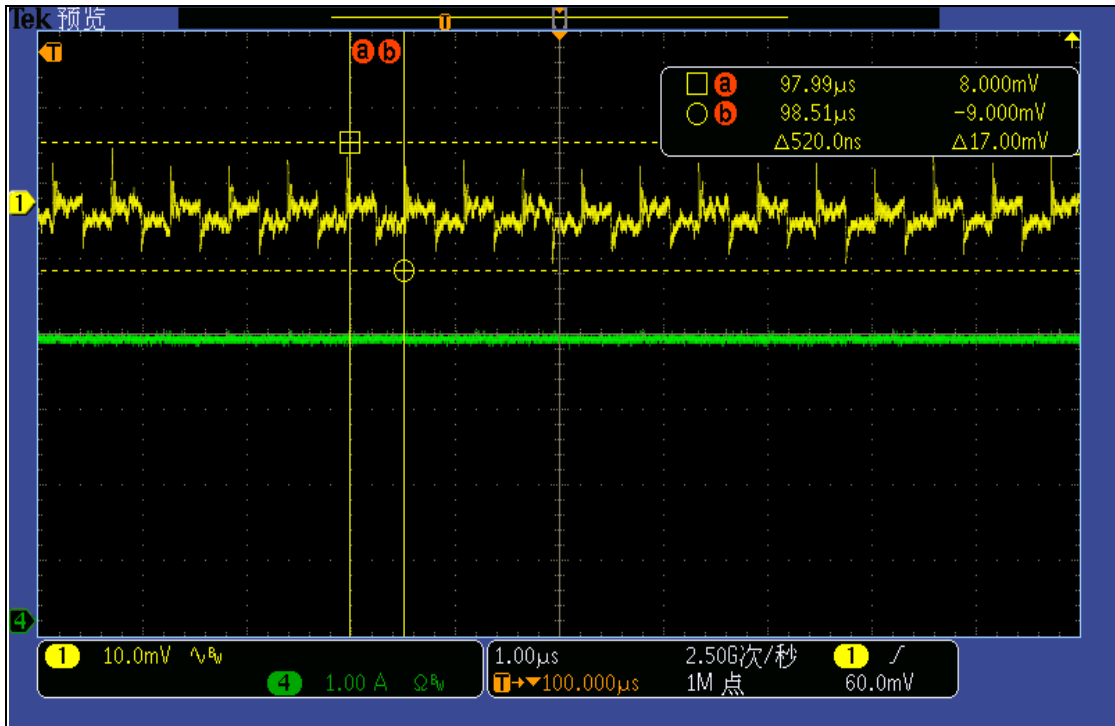


Vin:12Vdc Io: 4A
 Ch1: Output Ripple Voltage 10mV/div
 Ch3: Output Current 1A/div


2.1.3 Dynamic response:

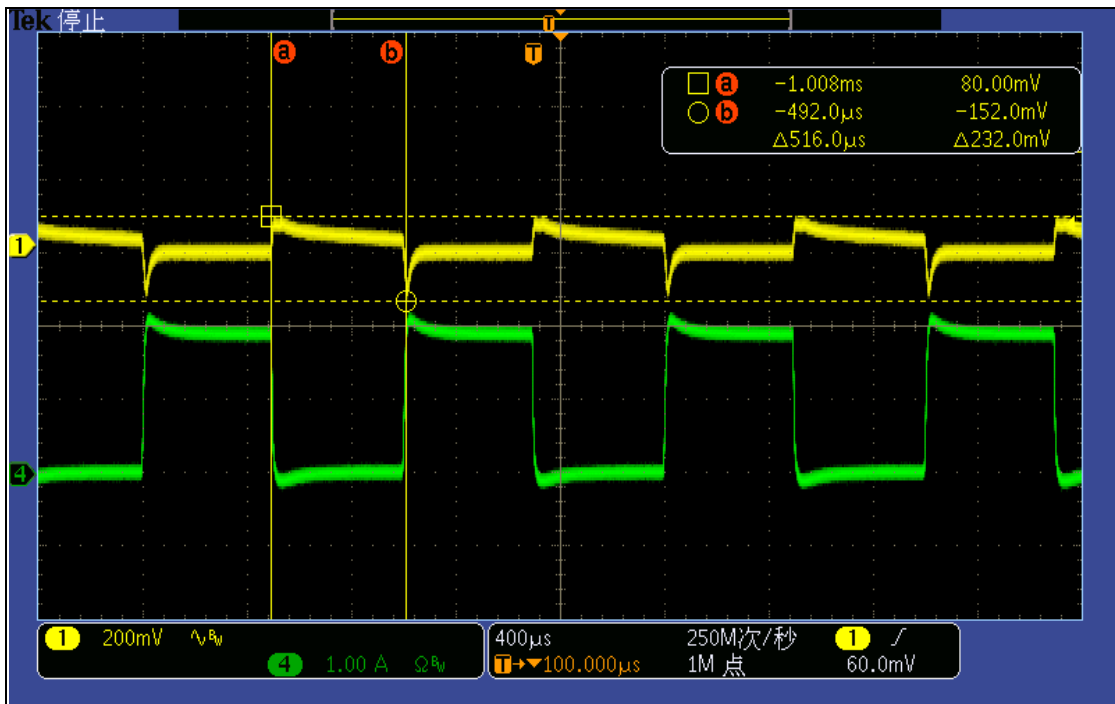

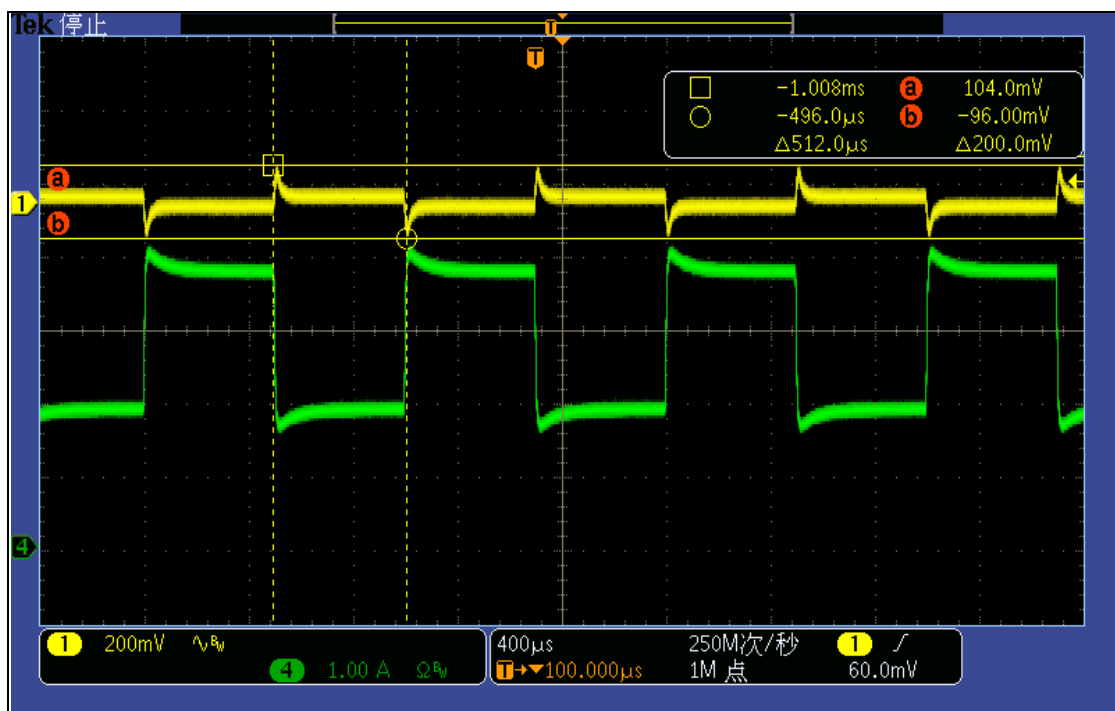Vin:12Vdc Io: 0A-2A 0.5mS, 2.5A/ μ S
 Ch1: Output Ripple Voltage 200mV/div
 Ch3: Output Current 1A/div



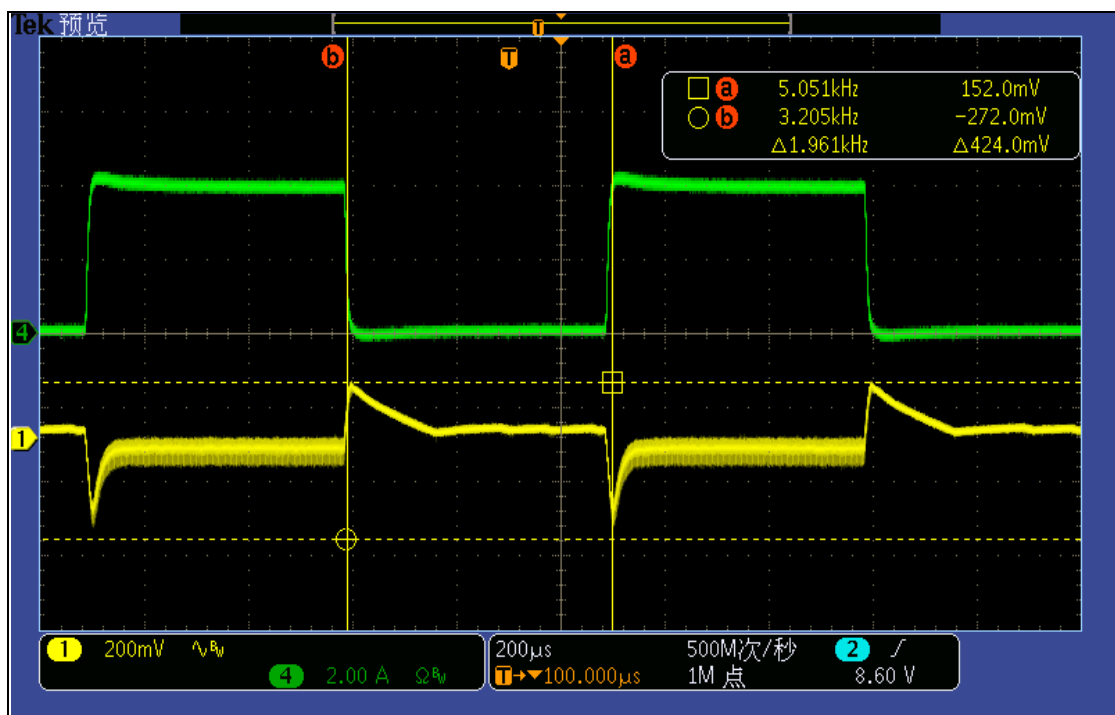Vin:12Vdc Io: 2A-4A 0.5mS, 2.5A/μS
 Ch1: Output Ripple Voltage 200mV/div
 Ch3: Output Current 1A/div




Vin:12Vdc Io: 0A-4A 0.5mS, 2.5A/μS
 Ch1: Output Ripple Voltage 200mV/div
 Ch4: Output Current 2A/div

2.2 TPS54388 for 1.5V/3A

2.2.1 Output regulation and curve:

12V	Output Current(A)	Output Voltage(V)
	No load	1.4975
	0.50	1.4948
	1.00	1.4930
	1.50	1.4915
	2.00	1.4900
	2.50	1.4885
	3.00	1.4871

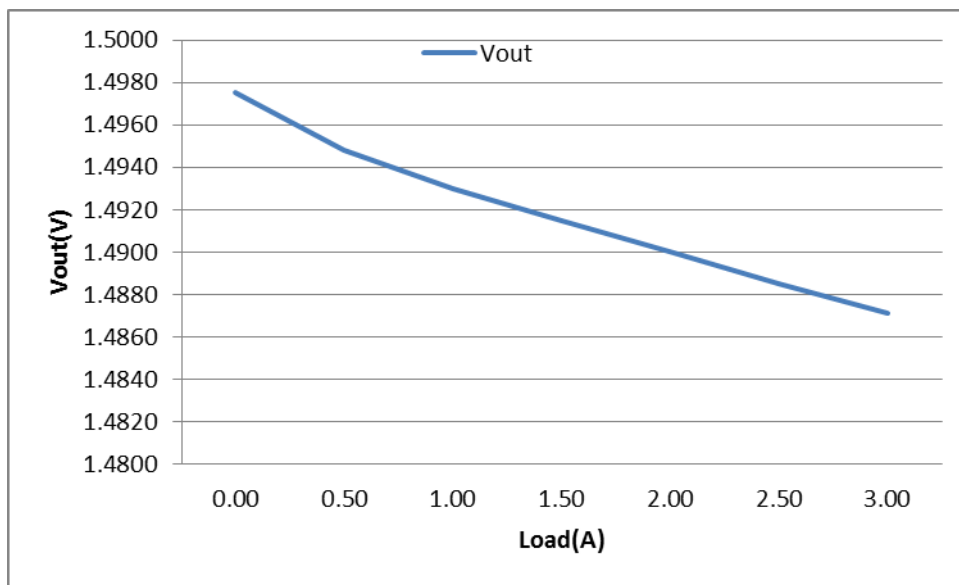


2.2.2 Output ripple voltage:




Vin:12Vdc Io: 3A
Ch1: Output Current 1A/div
Ch3: Output Ripple Voltage 10mV/div


2.2.3 Dynamic response:

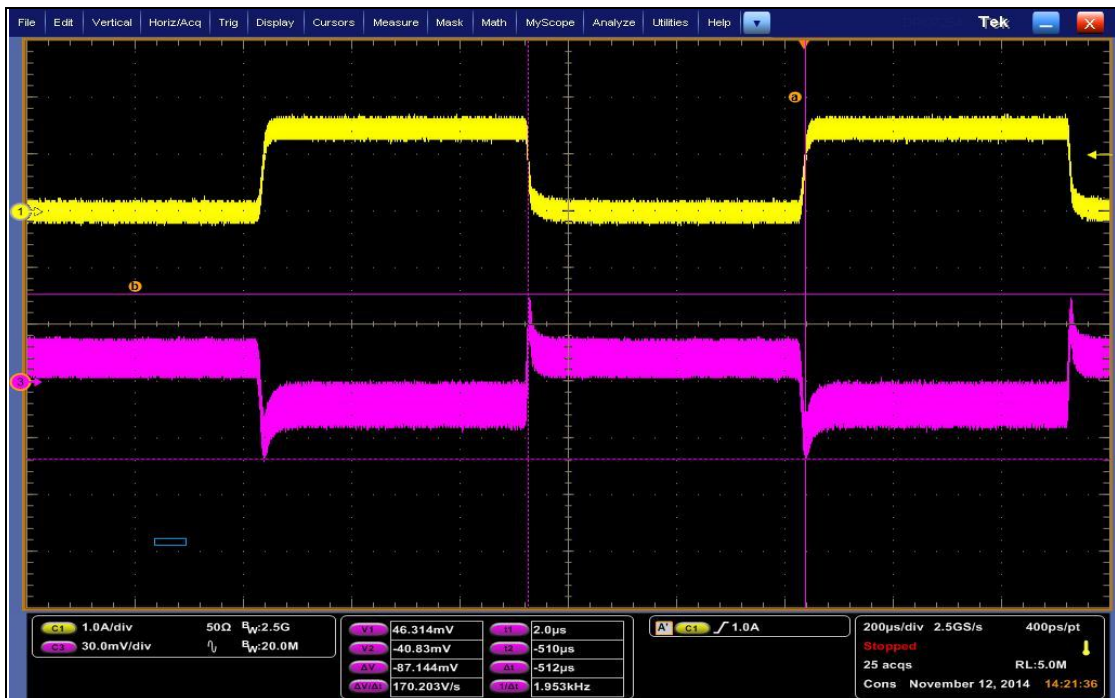

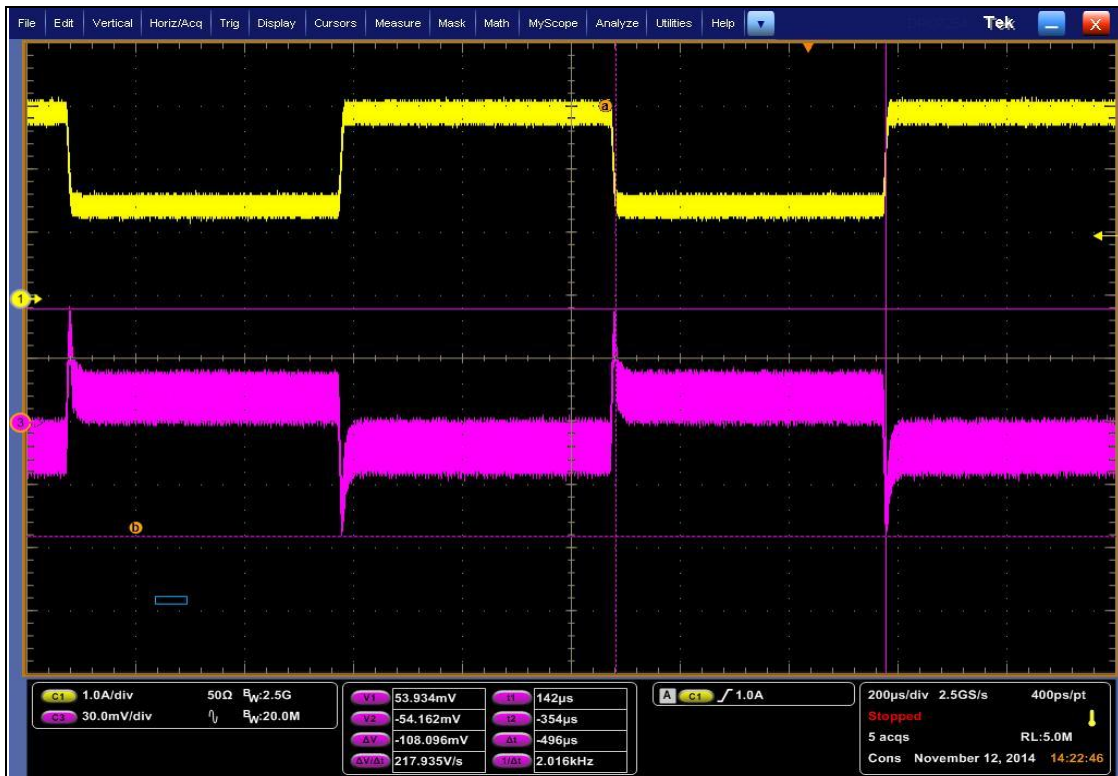Vin:12Vdc Io: 0A-1.5A 0.5mS, 2.5A/uS
Ch1: Output Current 1A/div
Ch3: Output Ripple Voltage 30mV/div



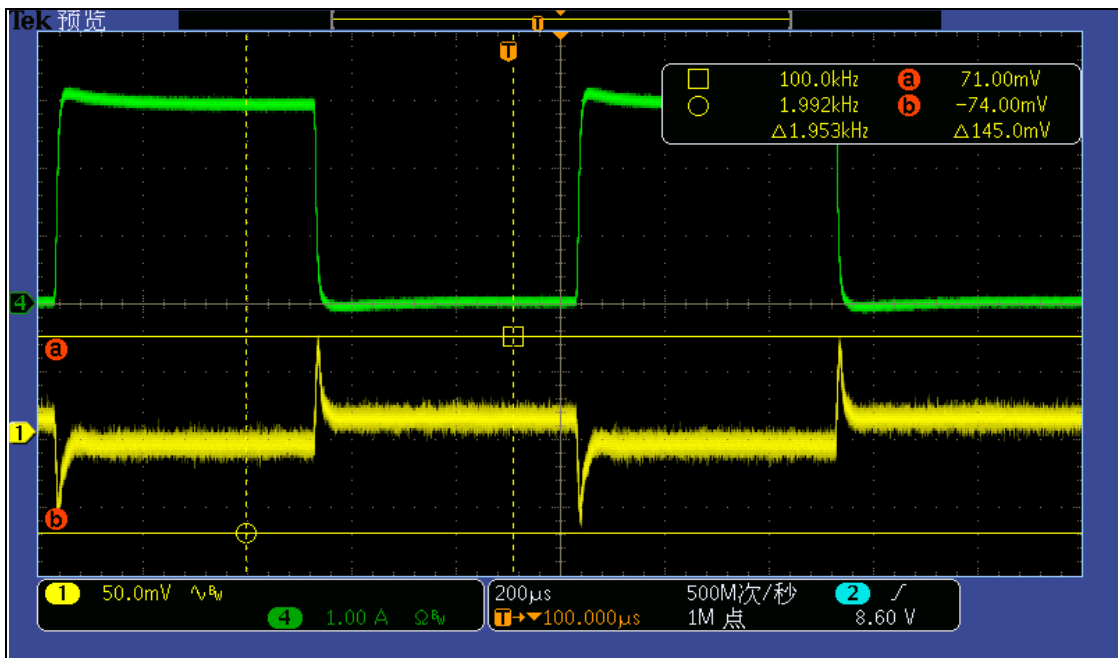Vin:12Vdc Io: 1.5A-3A 0.5mS, 2.5A/uS
 Ch1: Output Current 1A/div
 Ch3: Output Ripple Voltage 30mV/div




Vin:12Vdc Io: 0A-3A 0.5mS, 2.5A/uS
 Ch1: Output Ripple Voltage 50mV/div
 Ch4: Output Current 1A/div

2.3 TPS57114 for 1.425V/4A

2.3.1 Output regulation and curve:

12V	Output Current(A)	Output Voltage(V)
	No load	1.4251
	0.50	1.4237
	1.00	1.4227
	1.50	1.4219
	2.00	1.4211
	2.50	1.4203
	3.00	1.4195
	3.50	1.4188
	4.00	1.4181

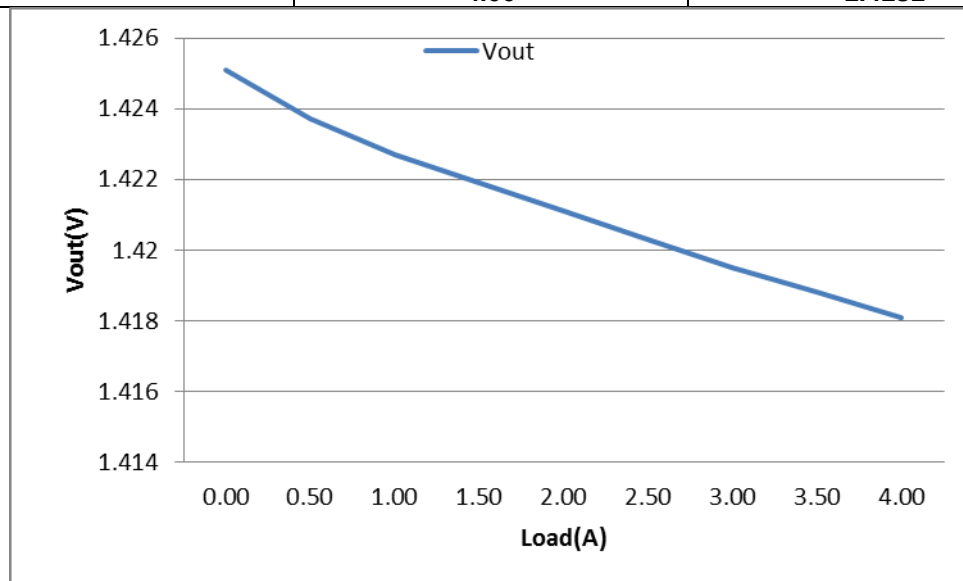


2.3.2 Output ripple voltage:



Vin:12Vin Io: 4A
 Ch1: Output Current 1A/div
 Ch3: Output Ripple Voltage 10mV/div


2.3.3 Dynamic response:

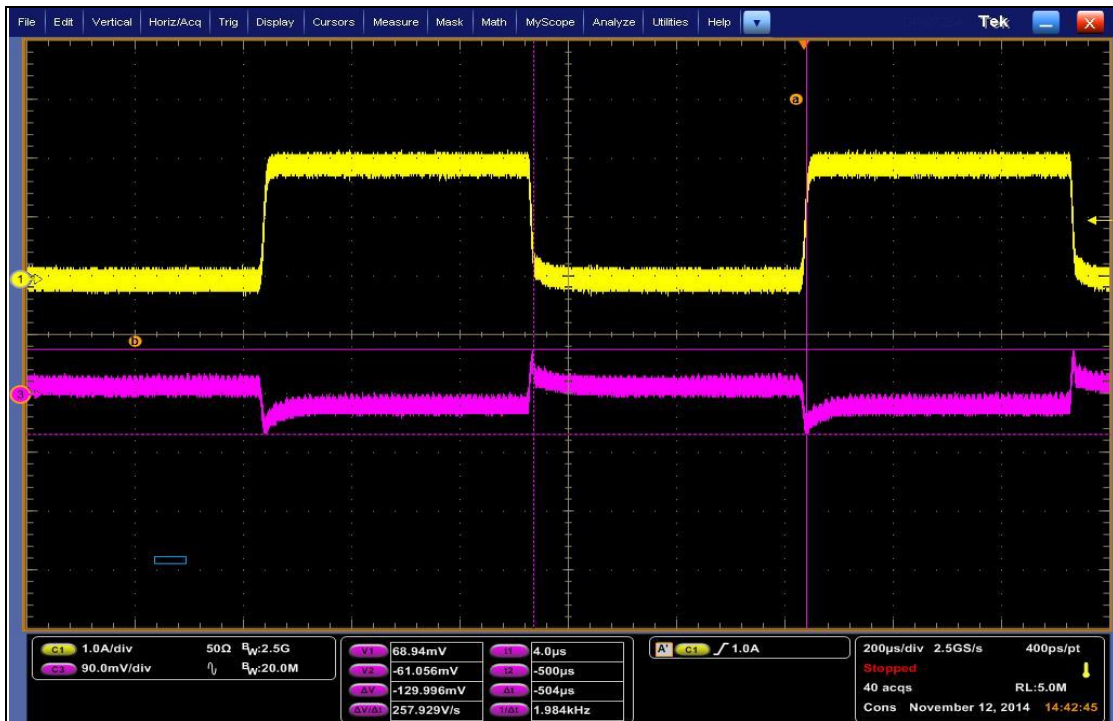

Vin:12Vdc Io: 0A-2A 0.5mS, 2.5A/uS
 Ch1: Output Current 1A/div
 Ch3: Output Ripple Voltage 90mV/div



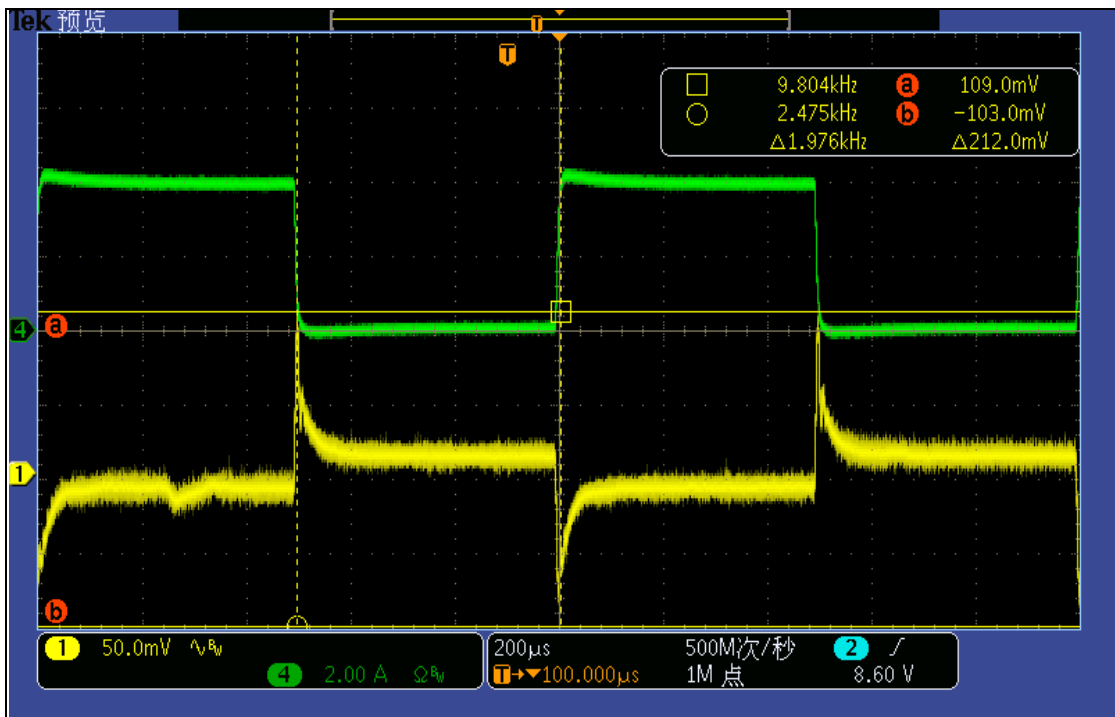Vin: 12Vdc Io: 2A-4A 0.5mS, 2.5A/μS
 Ch1: Output Current 1A/div
 Ch3: Output Ripple Voltage 30mV/div




Vin: 12Vdc Io: 0A-4A 0.5mS, 2.5A/μS
 Ch1: Output Ripple Voltage 50mV/div
 Ch4: Output Current 2A/div

2.4 LM26420 for 1.8V/1A

2.4.1 Output regulation and curve:

12V	Output Current(A)	Output Voltage(V)
	No load	1.8005
	0.20	1.8005
	0.40	1.8004
	0.60	1.8003
	0.80	1.8002
	1.00	1.8001

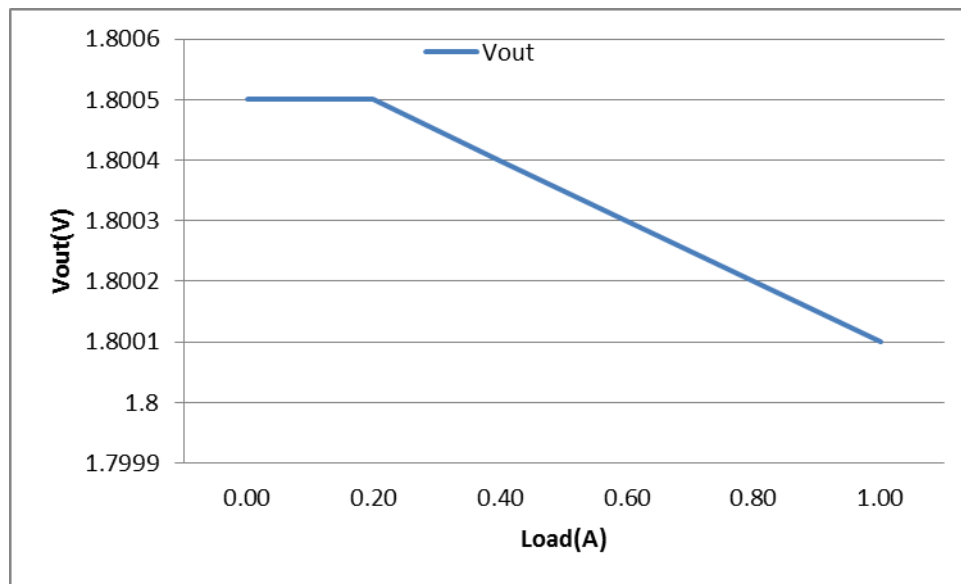

2.4.2 Output ripple voltage:



Vin:12Vin Io: 1A
 Ch1: Output Current 500mA/div
 Ch3: Output Ripple Voltage 10mV/div

2.4.3 Dynamic response:




Vin:12Vdc Io: 0A-0.5A 0.5mS, 2.5A/uS
 Ch1: Output Current 500mA/div
 Ch3: Output Ripple Voltage 30mV/div



Vin:12Vdc Io: 0.5A-1.0A 0.5mS, 2.5A/uS

Ch1: Output Current 500mA/div

Ch3: Output Ripple Voltage 30mV/div

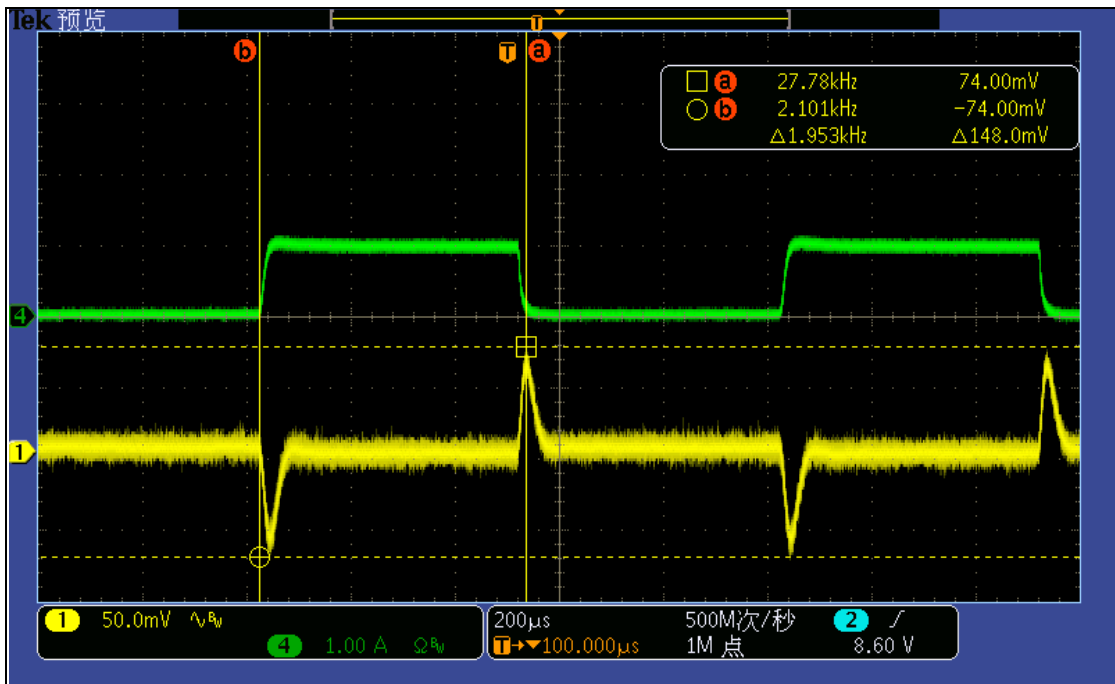

Vin:12Vdc Io: 0A-1A 0.5mS, 2.5A/uS


Ch1: Output Ripple Voltage 50mV/div

Ch4: Output Current 1A/div

2.5 LM26420 for 3.3V/1.5A

2.5.1 Output regulation and curve:

12V	Output Current(A)	Output Voltage(V)
	No load	3.3019
	0.30	3.3014
	0.60	3.3012
	0.90	3.3008
	1.20	3.3004
	1.50	3.3002

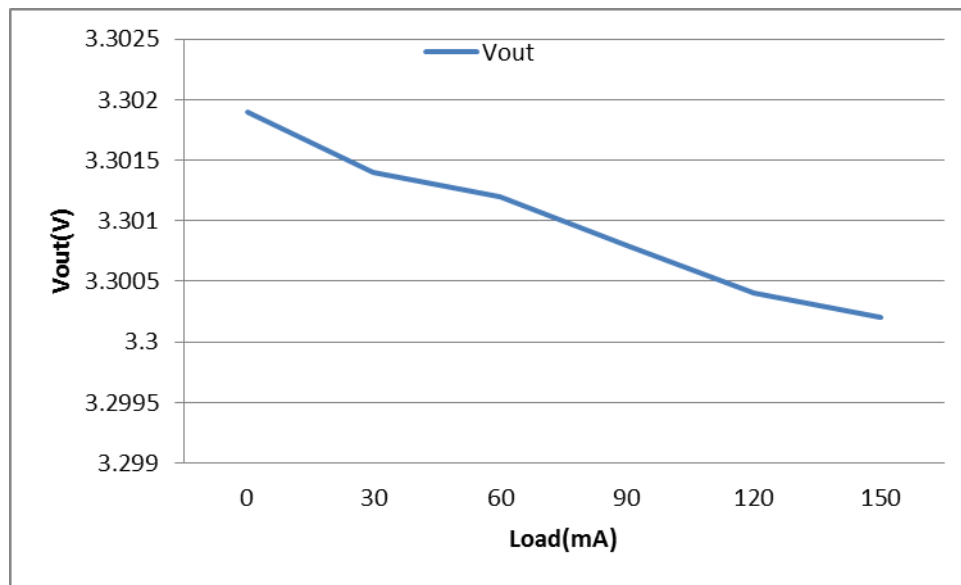

2.5.2 Output ripple voltage:



Vin:12Vin Io: 1.5A
Ch1: Output Current 500mA/div
Ch3: Output Ripple Voltage 10mV/div

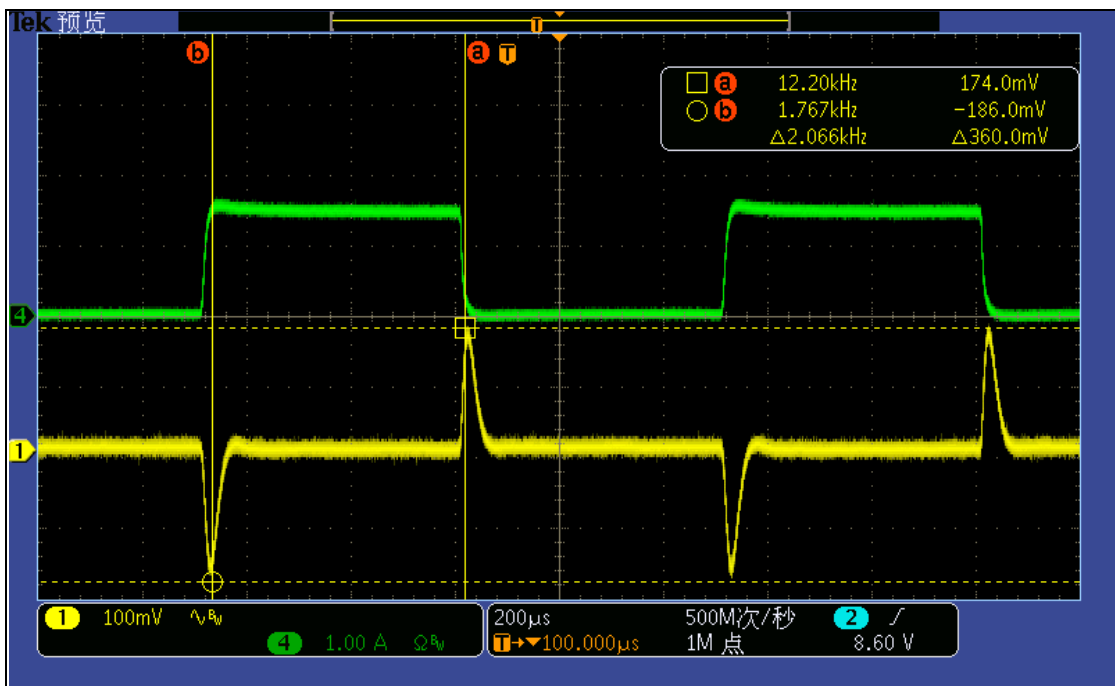
2.5.3 Dynamic response:



Vin:12Vdc Io: 0A-0.75A 0.5mS, 2.5A/μS
Ch1: Output Current 500mA/div
Ch3: Output Ripple Voltage 30mV/div



Vin:12Vdc Io: 0.75A-1.5A 0.5mS, 2.5A/μS
Ch1: Output Current 500mA/div
Ch3: Output Ripple Voltage 30mV/div




Vin:12Vdc Io: 0A-1.5A 0.5mS, 2.5A/μS
Ch1: Output Ripple Voltage 100mV/div
Ch4: Output Current 1A/div


2.6 TLV70030 for 3V/0.15A

2.6.1 Output regulation and curve:

12V	Output Current(A)	Output Voltage(V)
	No load	2.9913
	0.03	2.9915
	0.06	2.9917
	0.09	2.9918
	0.12	2.9918
	0.15	2.9921

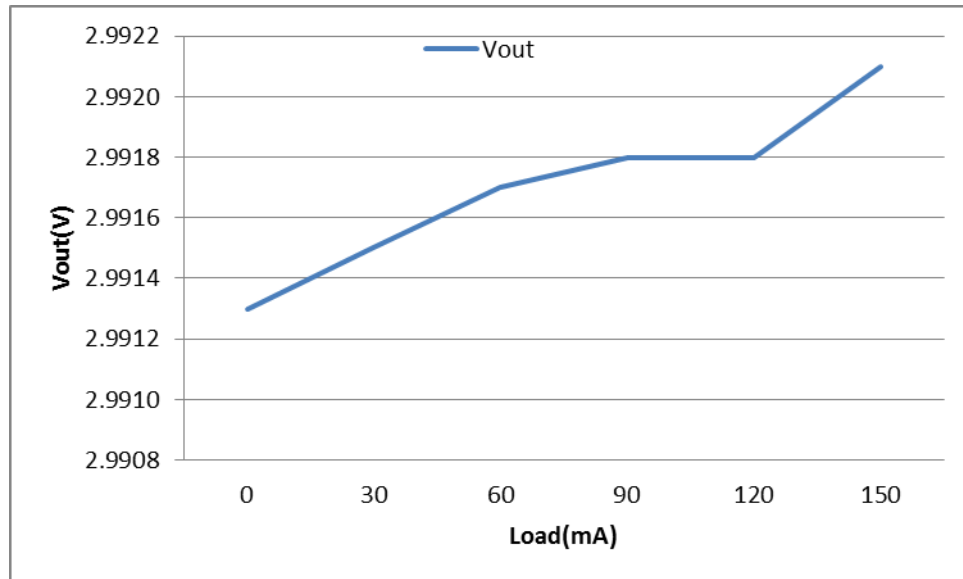



2.6.2 Output ripple voltage:

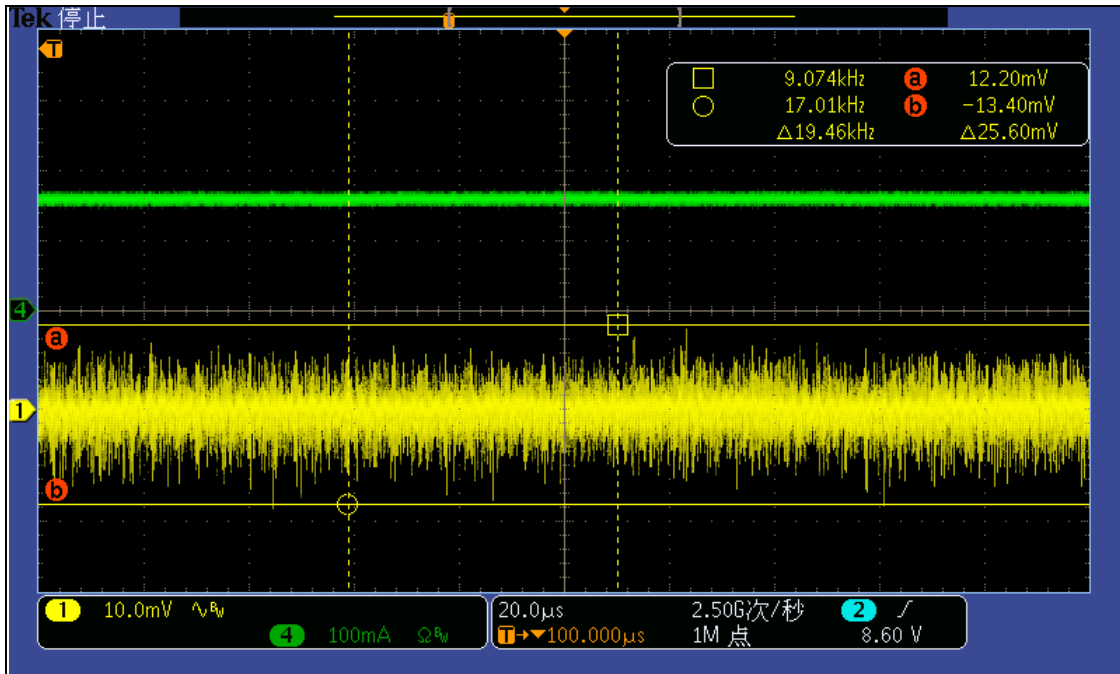

Vin:12Vin Io: 0.15A
 Ch1: Output Ripple Voltage 10mV/div
 Ch4: Output Current 100mA/div

3 Output Voltage Time Sequence

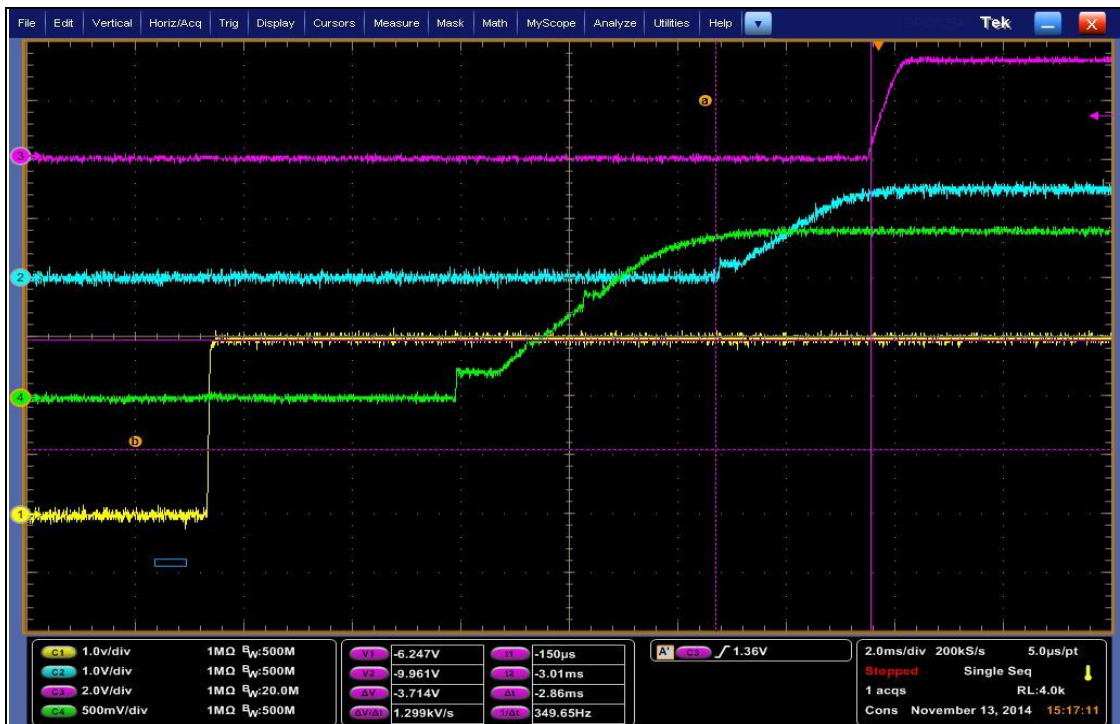

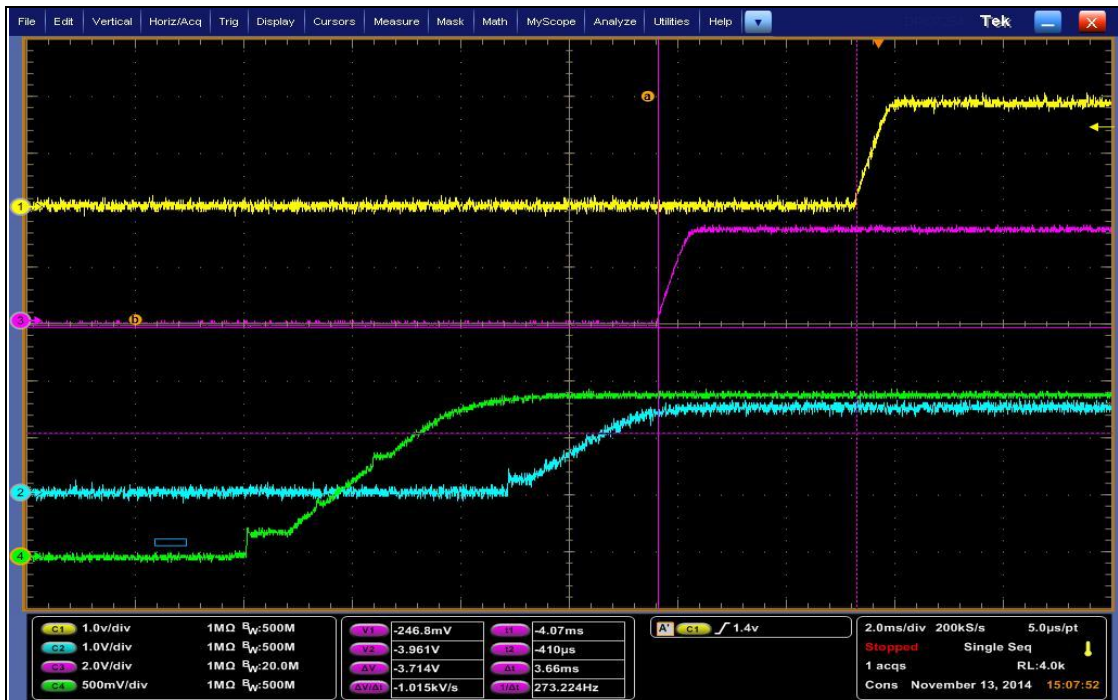


Vin:12Vdc

Ch1: 1.8V Output Voltage 1V/div Ch2: 1.425V Output Voltage 1V/div

Ch3: 3.3V Output Voltage 2V/div Ch4: 1.425V Output Voltage 500mV/div

4 Thermal performance

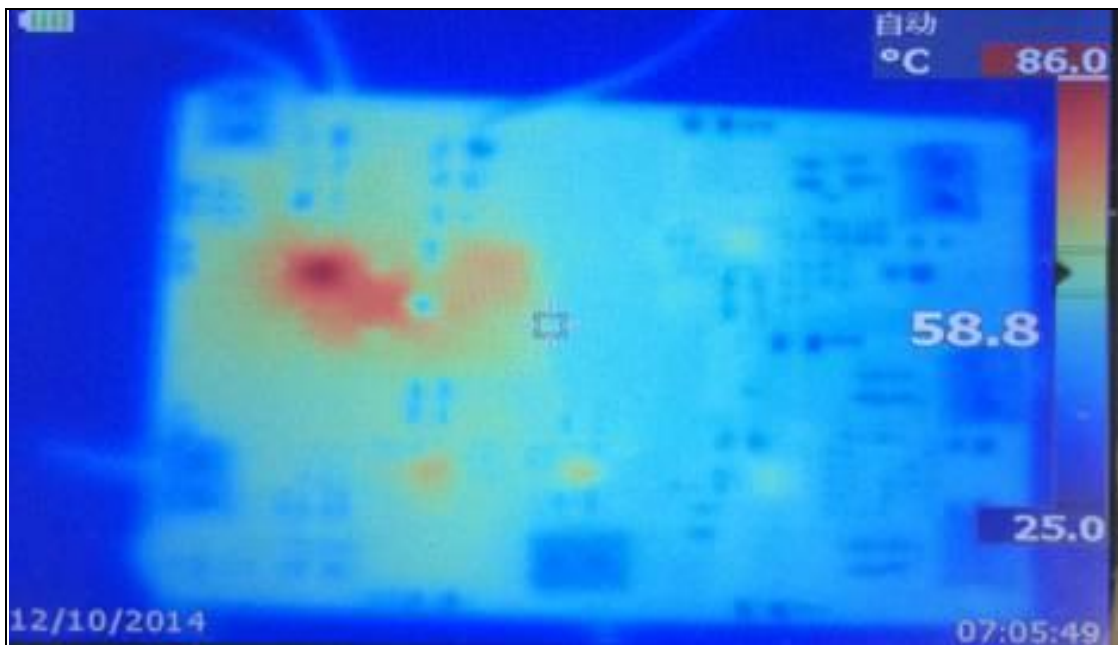

Vin:12Vdc TPS54388 Io: 1.5V/3A, TPS54388 Io: 1.425/4A, LM26420: 3.3V1.5A, 1.8V/1A, TLV70030 3V/0.15A

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated